

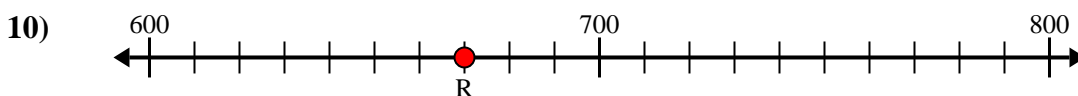
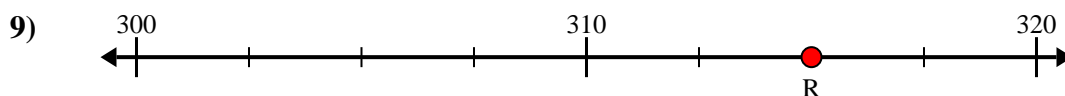
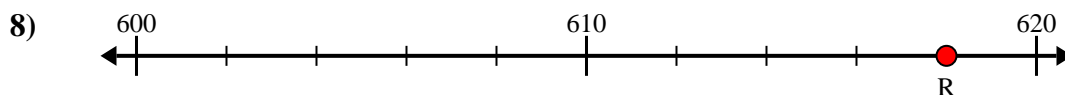
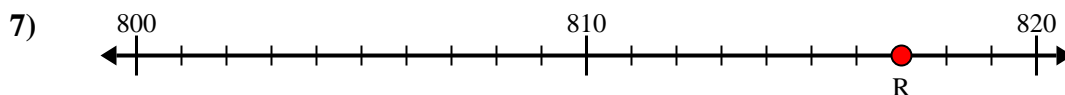
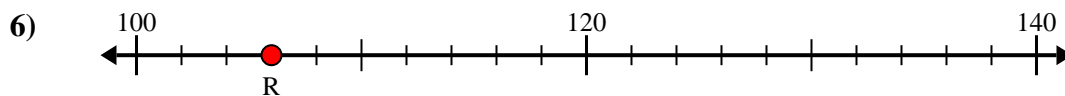
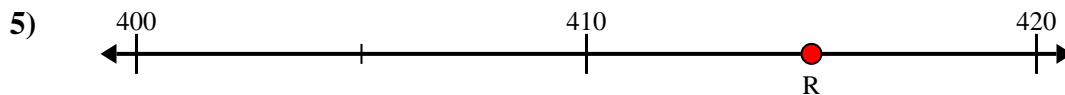
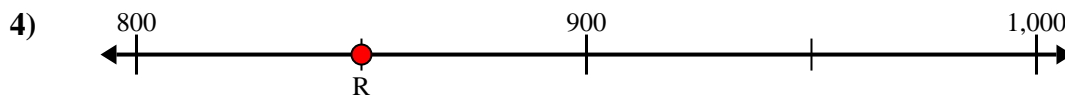
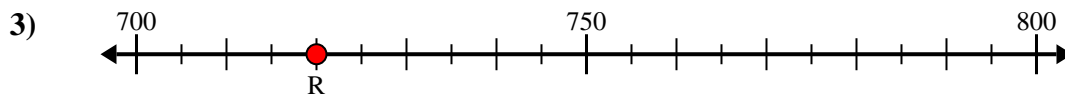


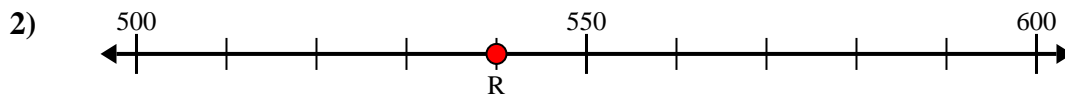

Trova il valore di R.

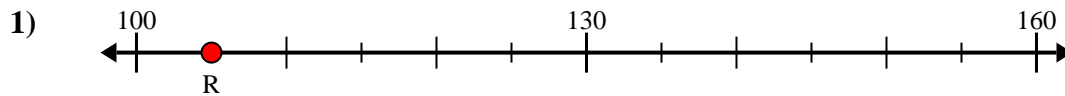

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

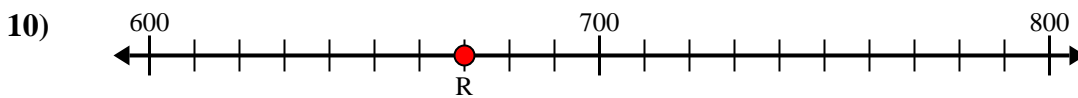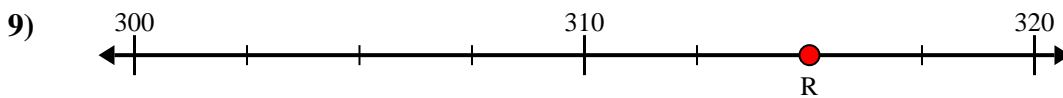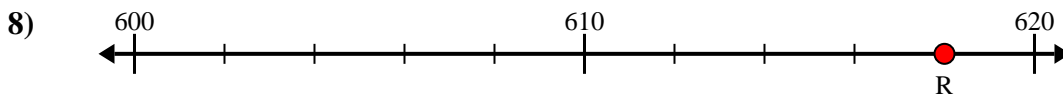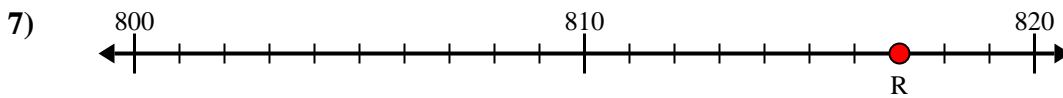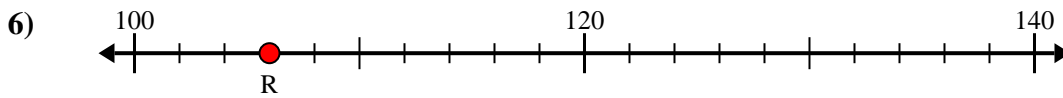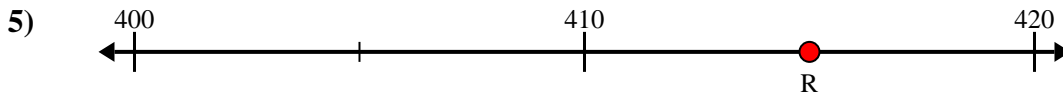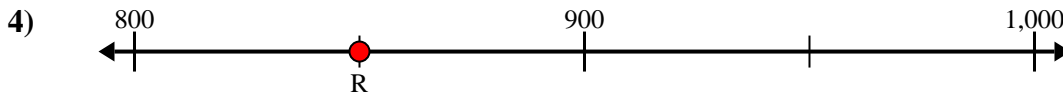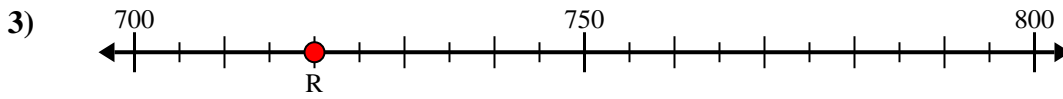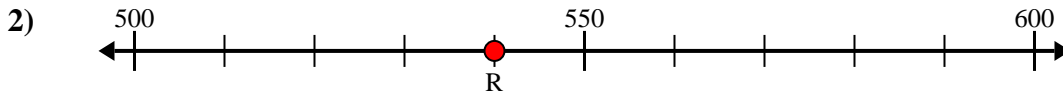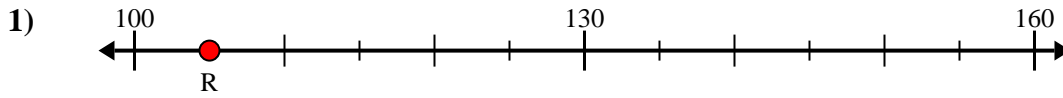

Risposte

1. 105

2. 540

3. 720

4. 850

5. 415

6. 106

7. 817

8. 618

9. 315

10. 670