

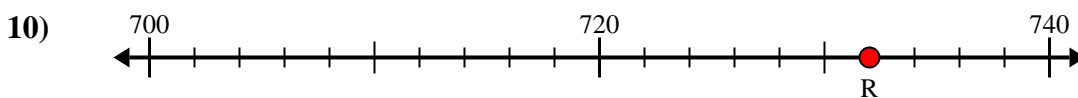
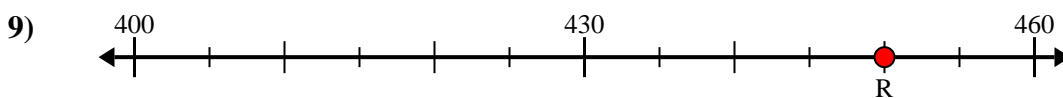
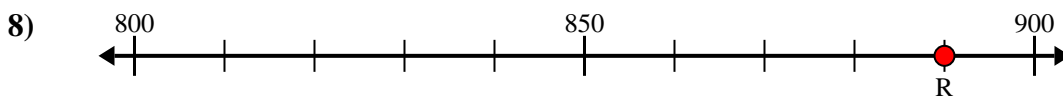
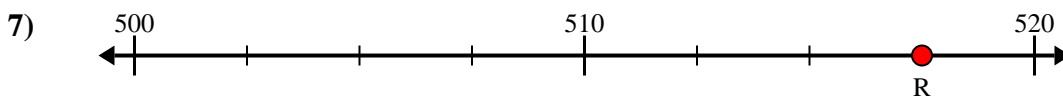
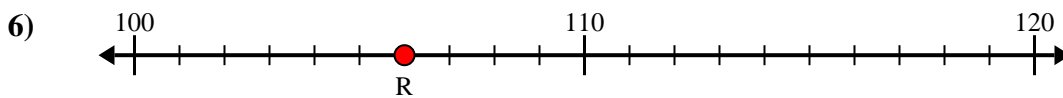
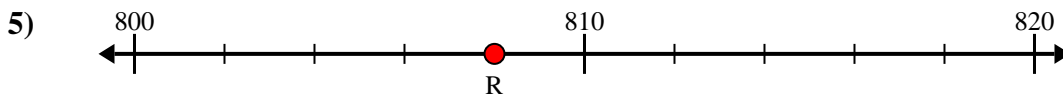
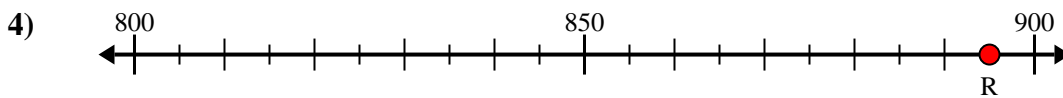
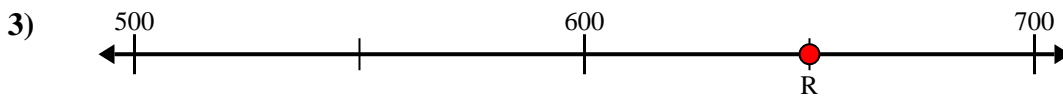


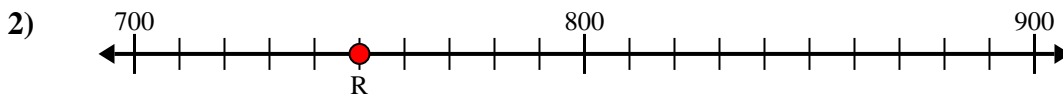

Trova il valore di R.

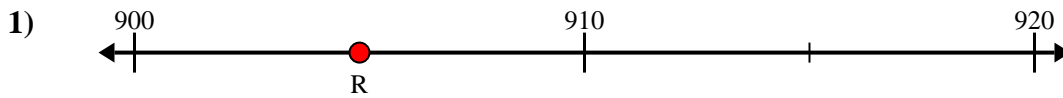

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

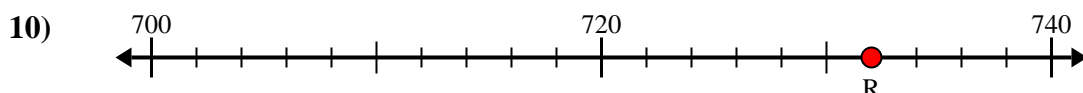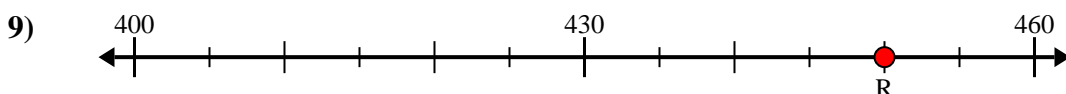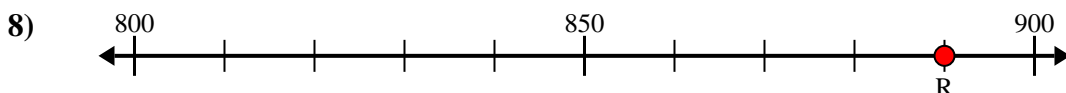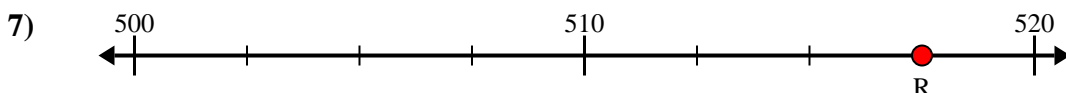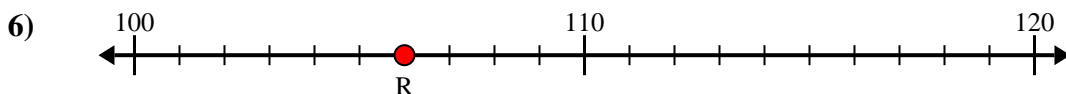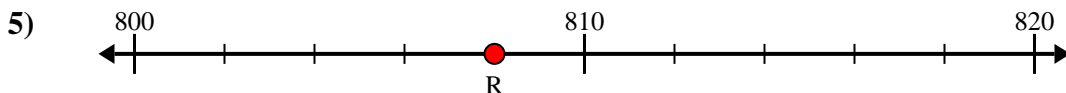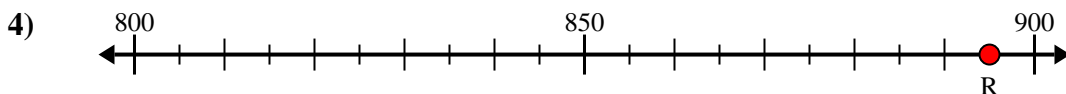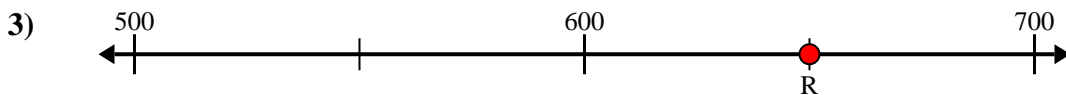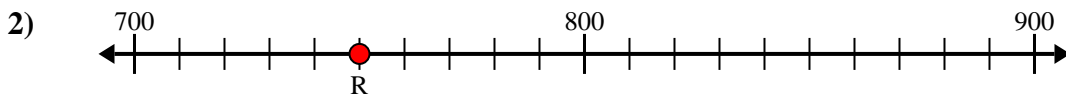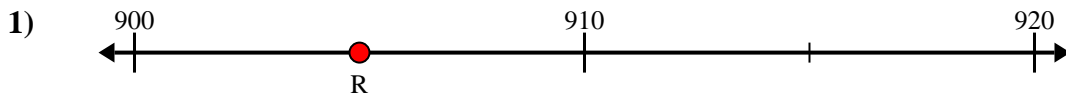

Risposte

1. 905

2. 750

3. 650

4. 895

5. 808

6. 106

7. 517.5

8. 890

9. 450

10. 732