

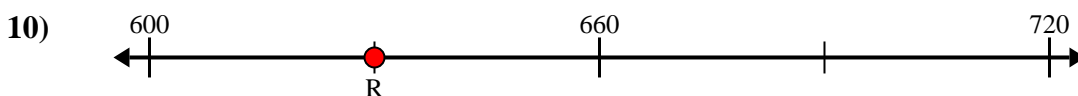
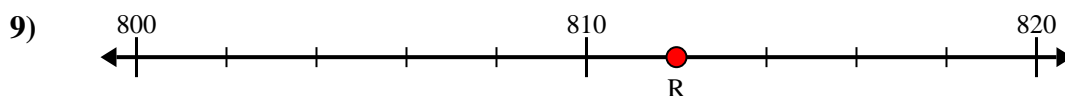
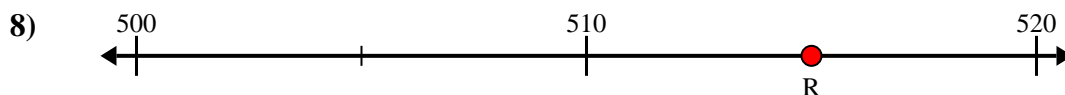
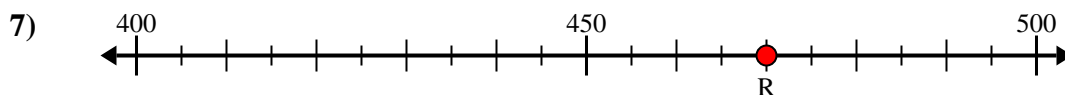
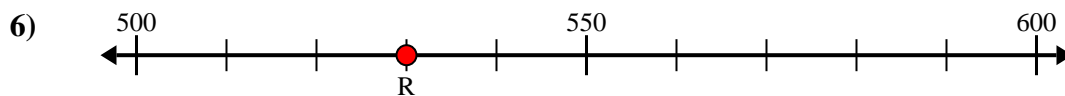
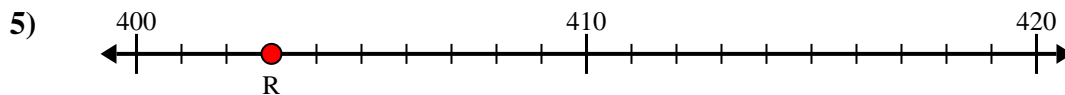
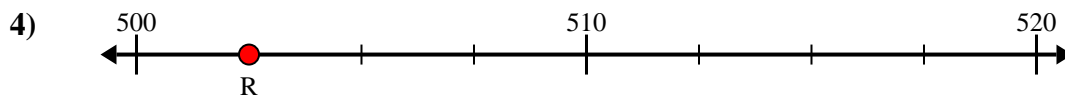
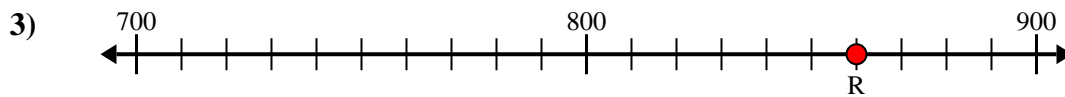


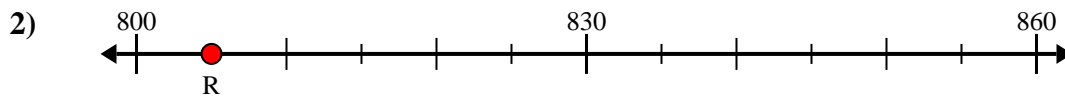

Trova il valore di R.

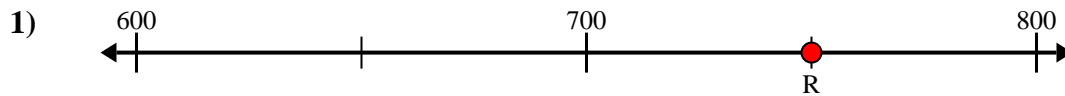

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

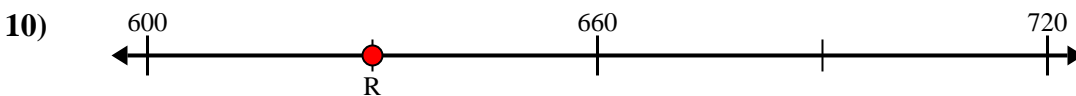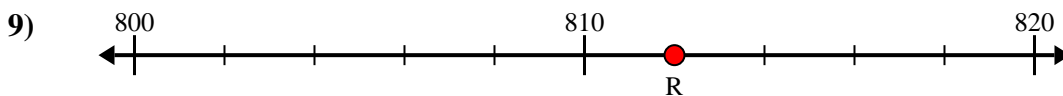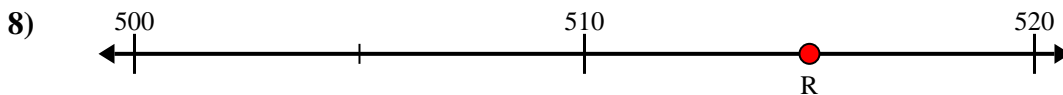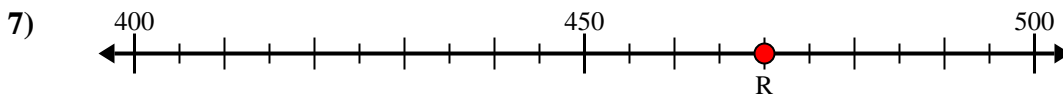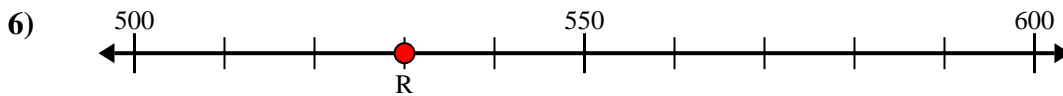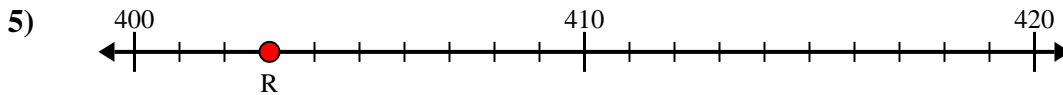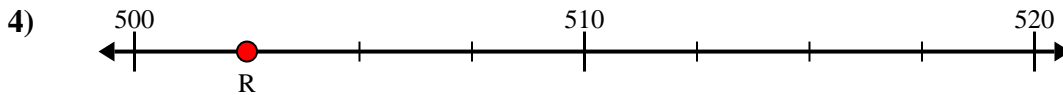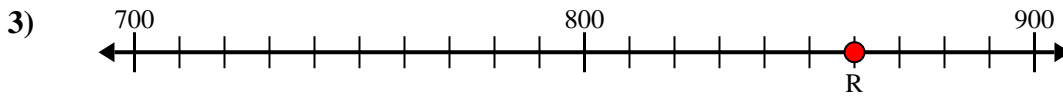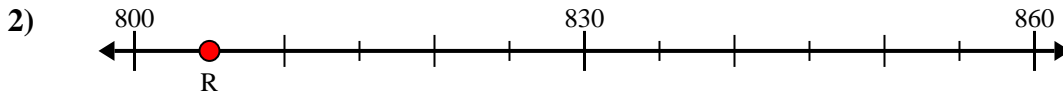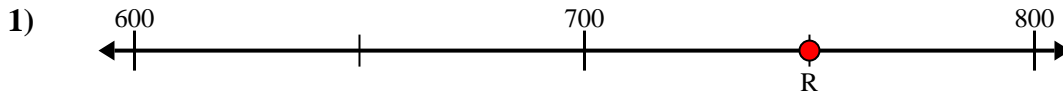

Risposte

1. 750

2. 805

3. 860

4. 502.5

5. 403

6. 530

7. 470

8. 515

9. 812

10. 630