

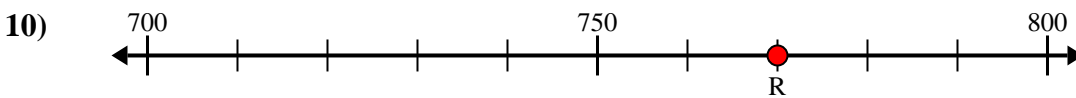
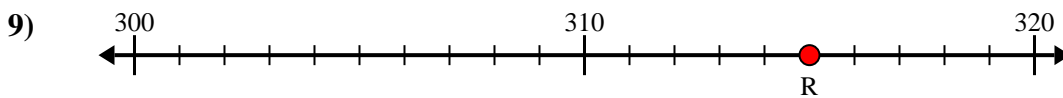
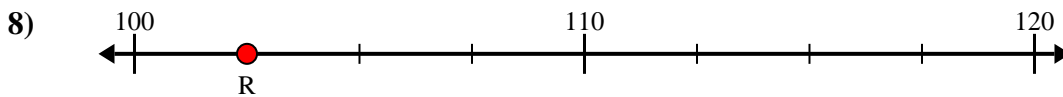
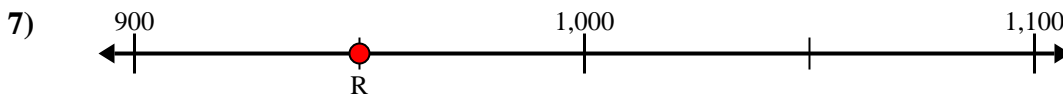
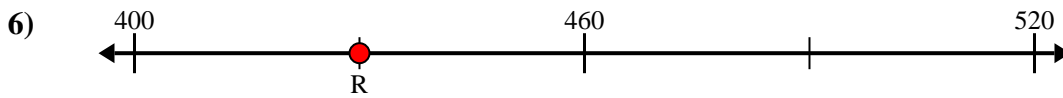
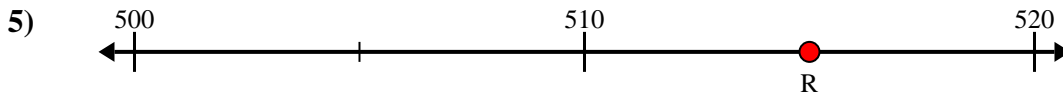
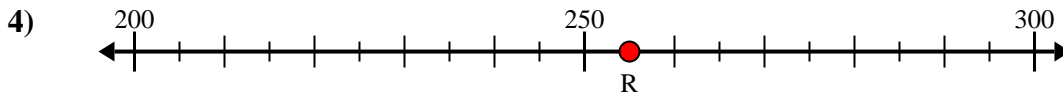
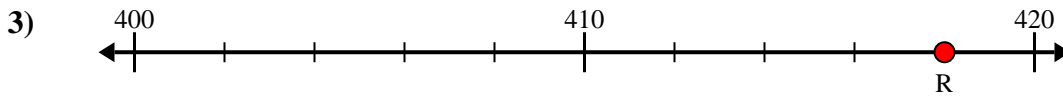


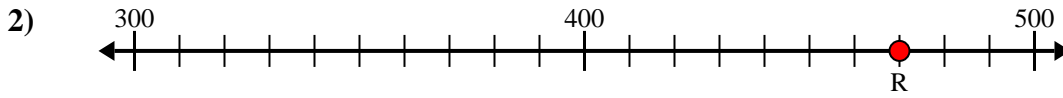

Trova il valore di R.

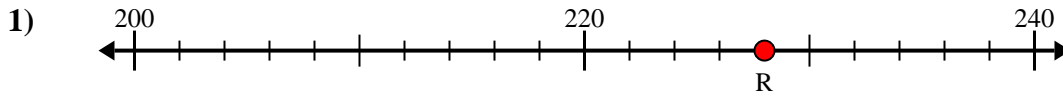

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

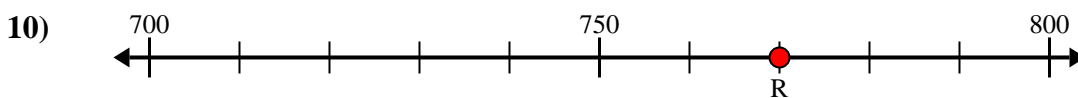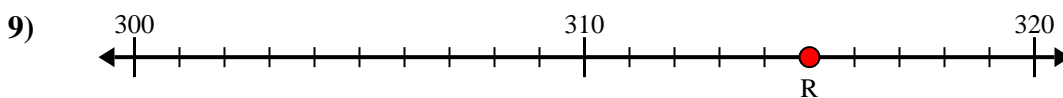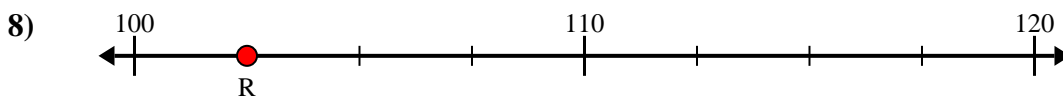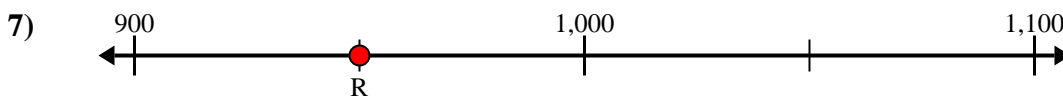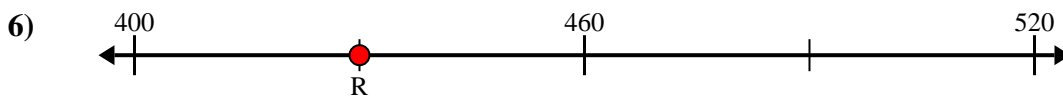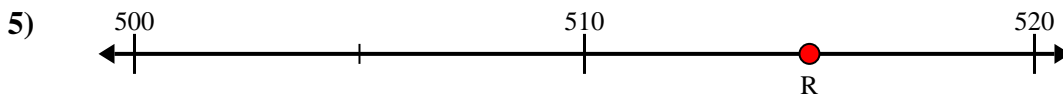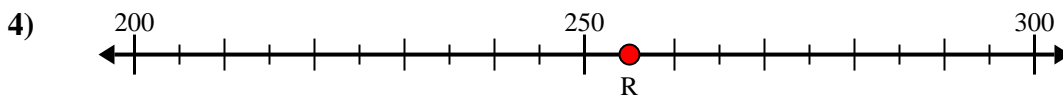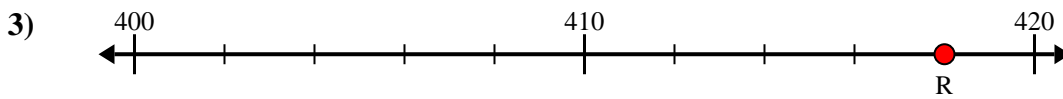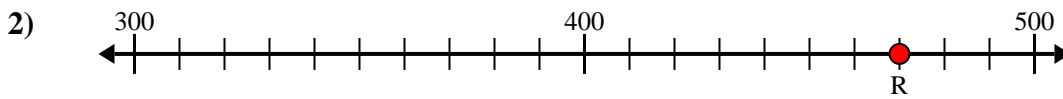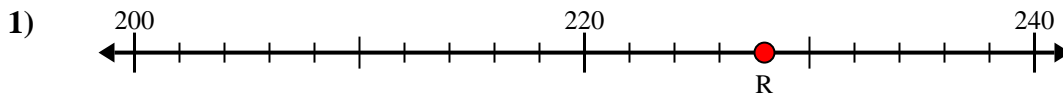

Risposte

1. 228

2. 470

3. 418

4. 255

5. 515

6. 430

7. 950

8. 102.5

9. 315

10. 770