

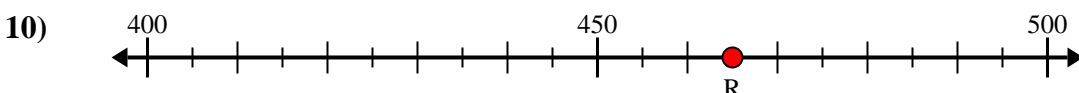
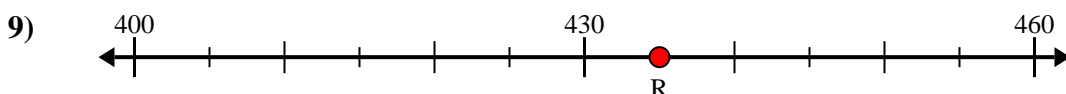
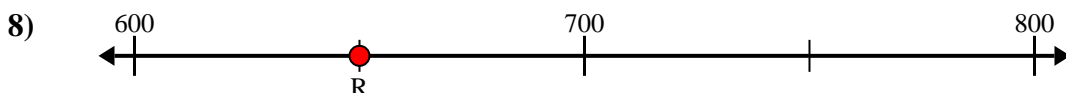
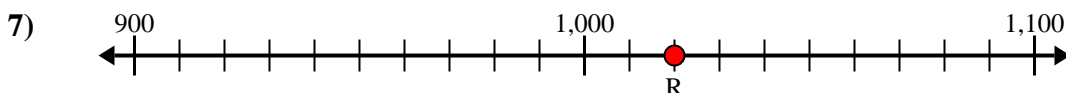
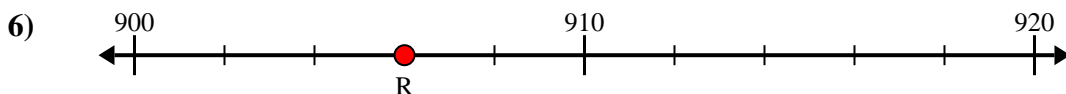
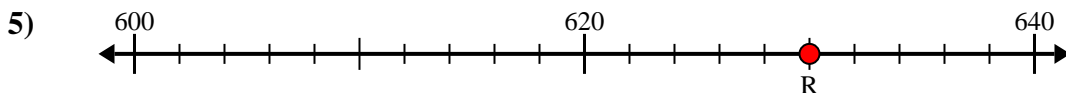
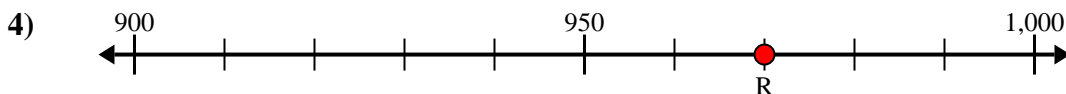
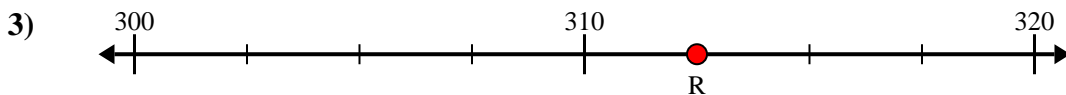


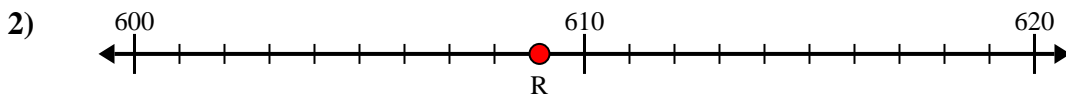

Trova il valore di R.

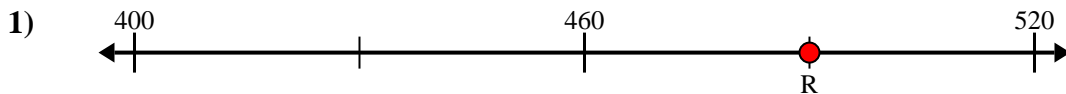

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

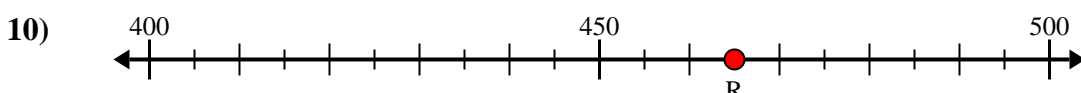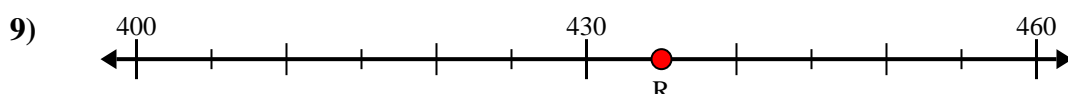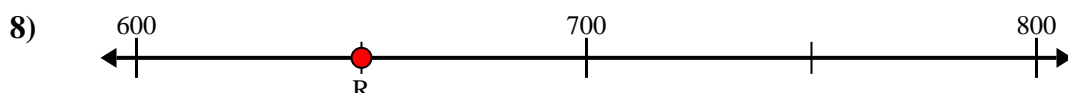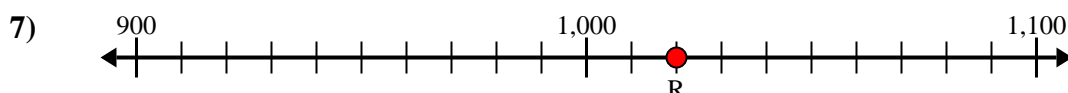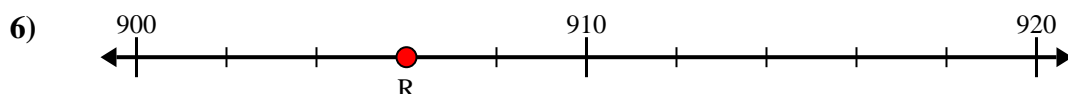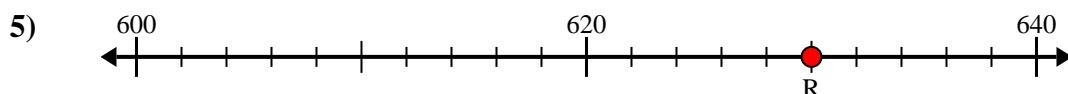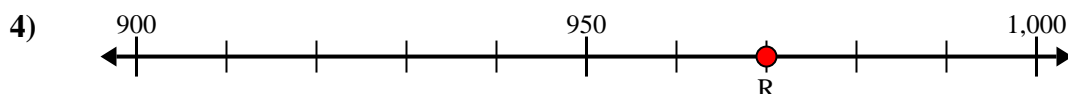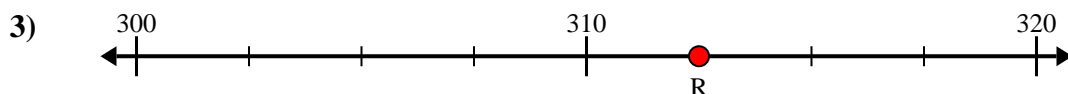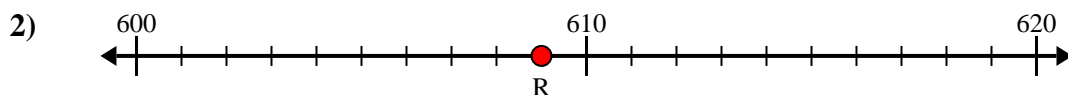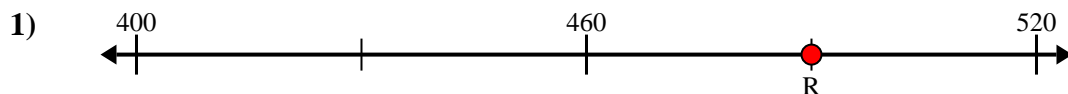

Risposte

1. 490

2. 609

3. 312.5

4. 970

5. 630

6. 906

7. 1,020

8. 650

9. 435

10. 465