

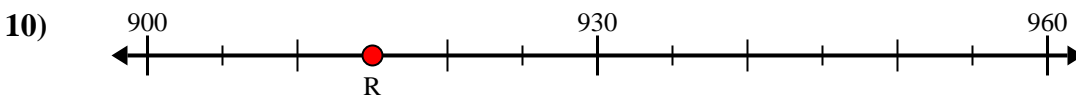
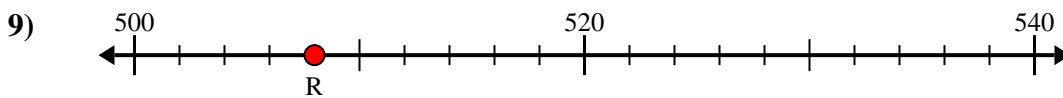
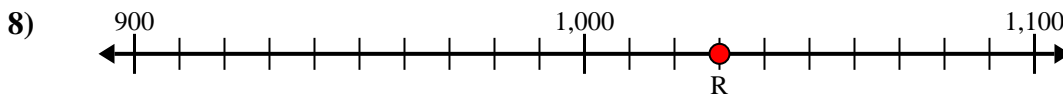
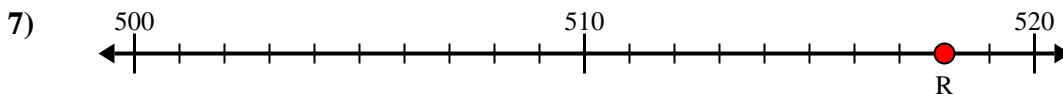
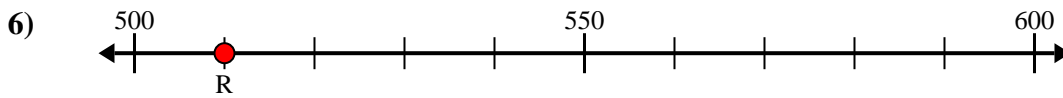
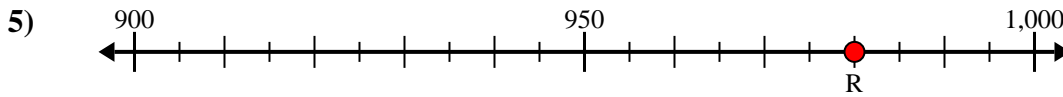
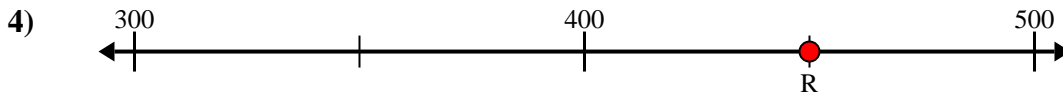
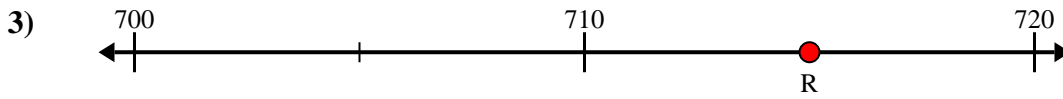


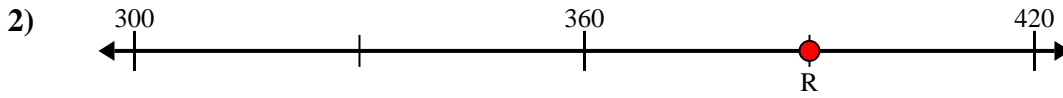

Trova il valore di R.

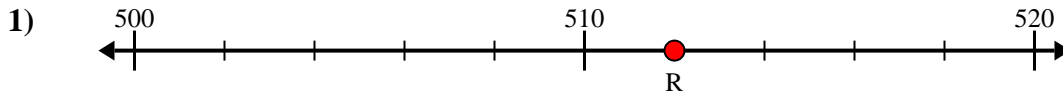

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

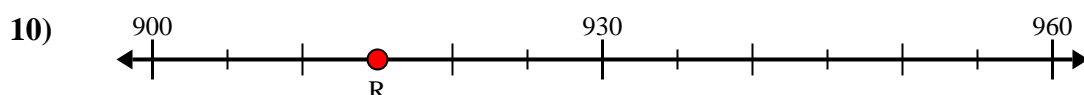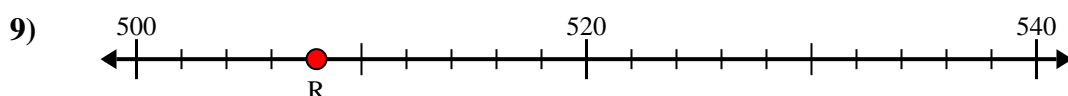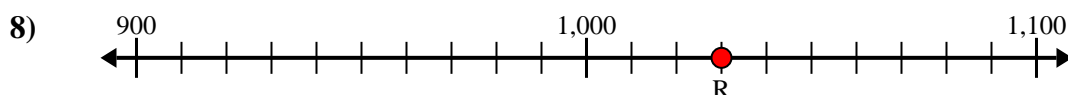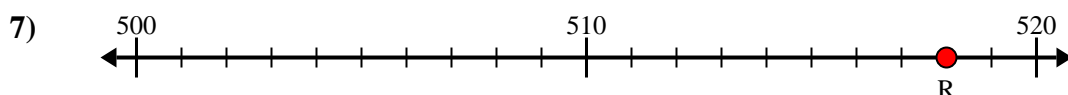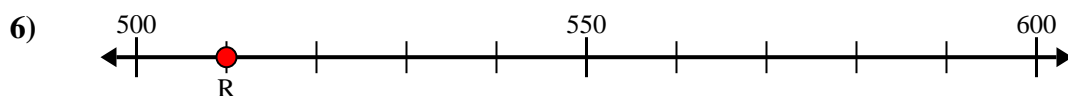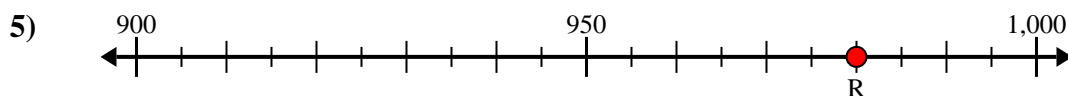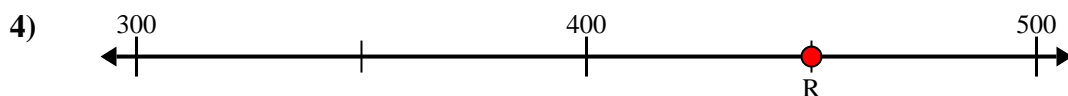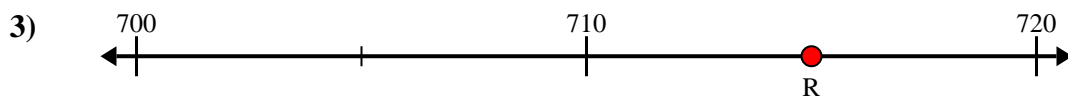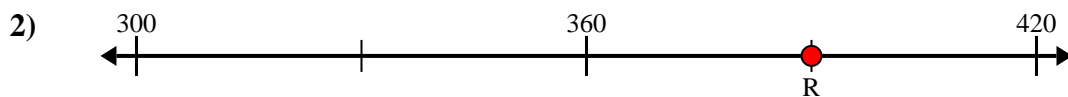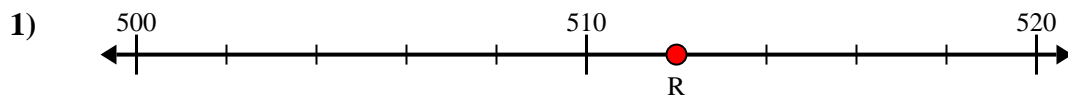

Risposte

1. 512

2. 390

3. 715

4. 450

5. 980

6. 510

7. 518

8. 1,030

9. 508

10. 915