

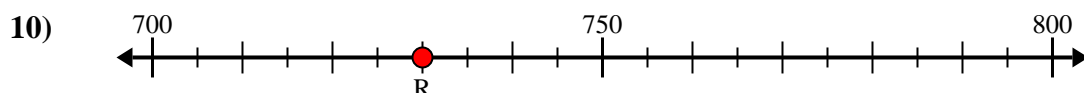
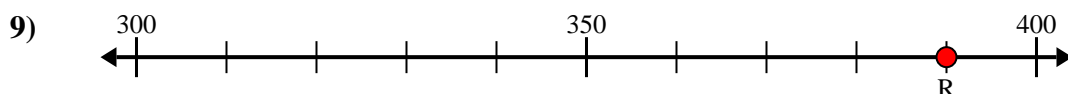
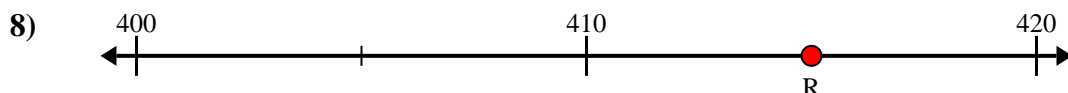
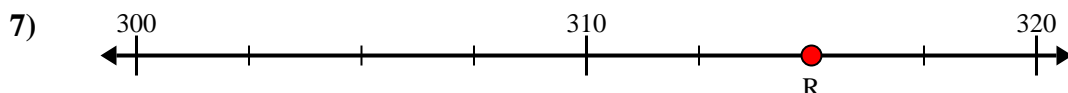
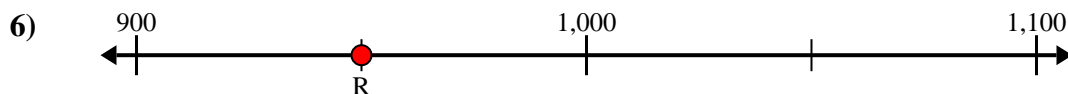
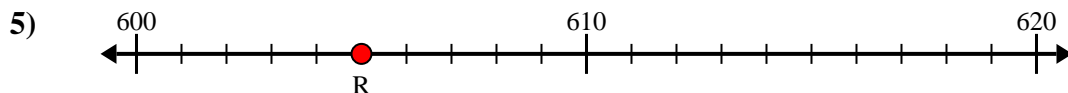
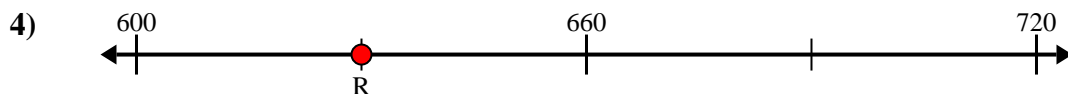
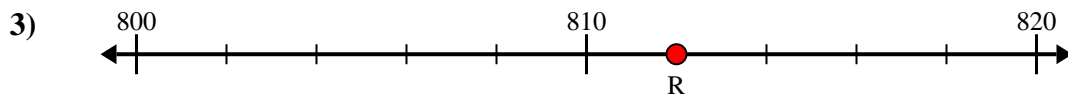


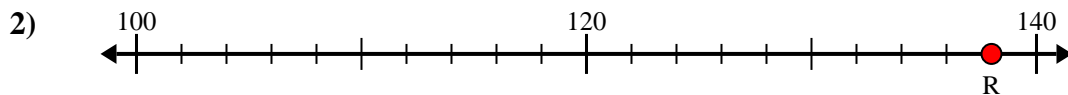

Trova il valore di R.

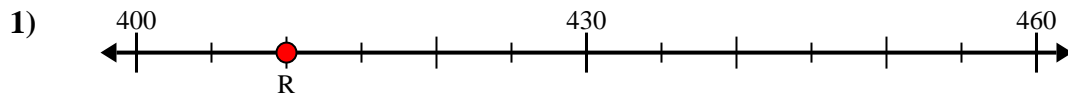

Risposte

1. _____

2. _____

3. _____

4. _____

5. _____

6. _____

7. _____











8. _____

9. _____

10. _____



Trova il valore di R.

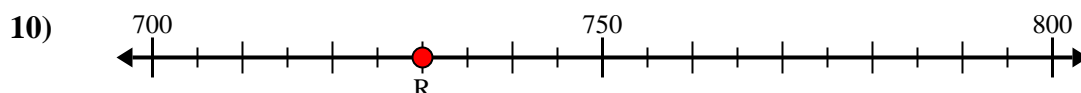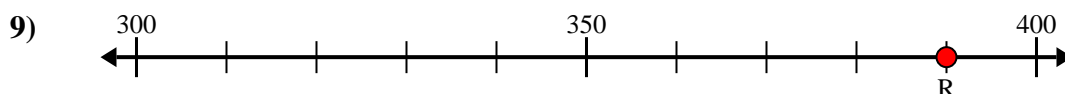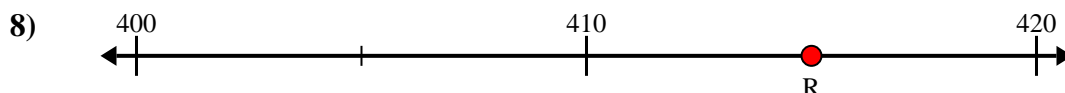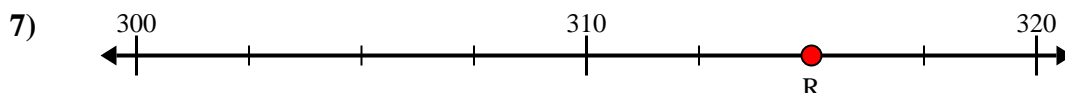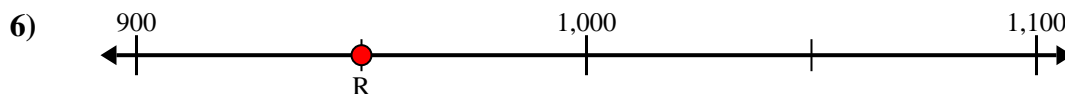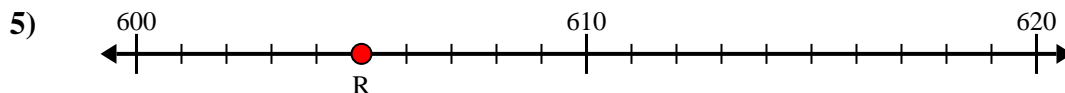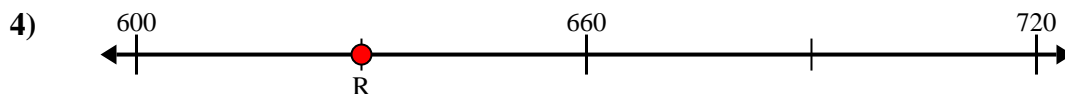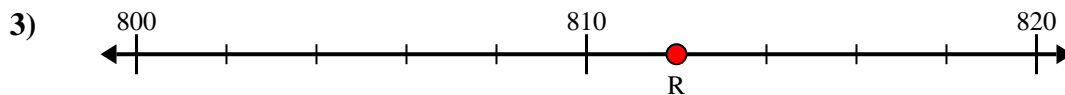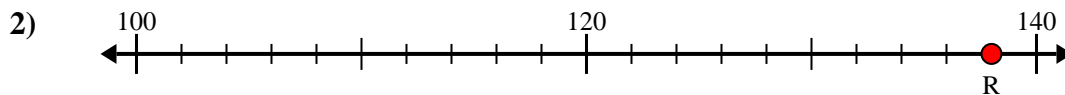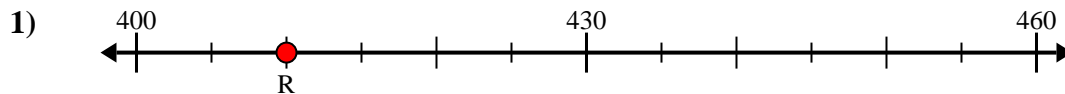

Risposte

1. 410

2. 138

3. 812

4. 630

5. 605

6. 950

7. 315

8. 415

9. 390

10. 730